

EE430 Electromagnetism
Project 5: Electric Field Strength Meter
May 7, 2025



- Cameron deLeeuw

Circuit Schematic:

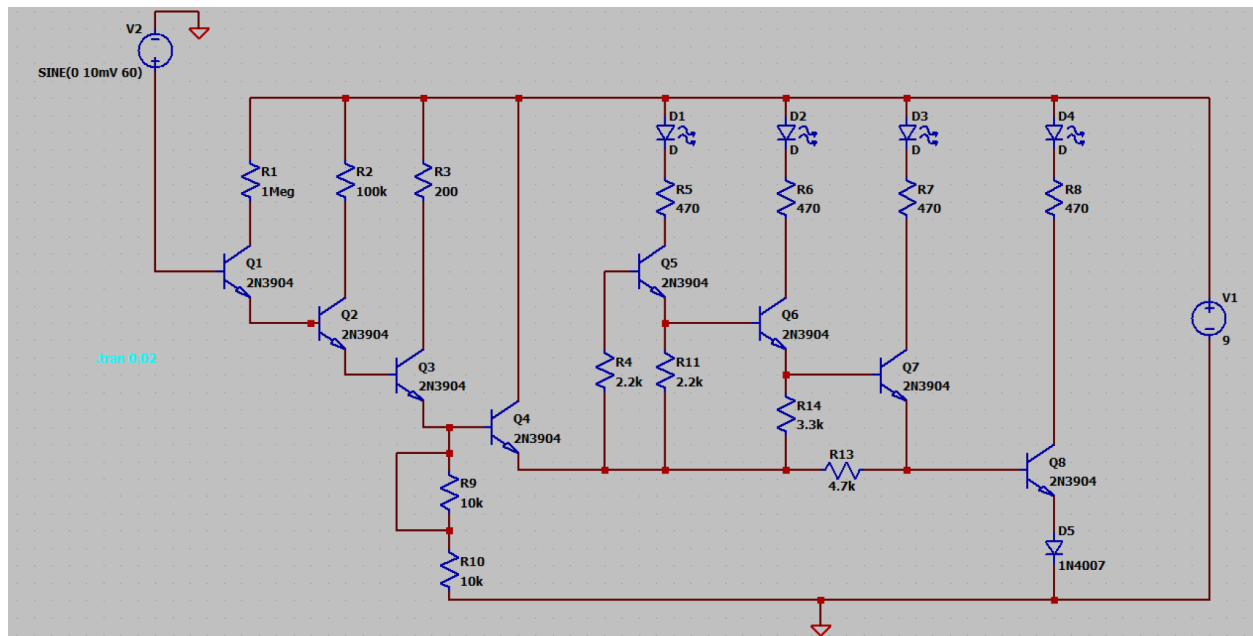


Fig.1

LTSpice Simulation:

- LED Currents with $R_{10} = 1k\Omega$:
 - $I_{D1} = 8.3 \text{ pA}$
 - $I_{D2} = 8.3 \text{ pA}$
 - $I_{D3} = 8.3 \text{ pA}$
 - $I_{D4} = 10.4 \text{ nA}$
- LED Currents with $R_{10} = 10k\Omega$:
 - $I_{D1} = 8.4 \text{ pA}$
 - $I_{D2} = 8.4 \text{ pA}$
 - $I_{D3} = 8.4 \text{ pA}$
 - $I_{D4} = 10.5 \text{ nA}$
- LED Currents with $R_{10} = 19k\Omega$:
 - $I_{D1} = 8.4 \text{ pA}$
 - $I_{D2} = 8.4 \text{ pA}$
 - $I_{D3} = 8.4 \text{ pA}$
 - $I_{D4} = 10.5 \text{ nA}$

Annotated Photo of the Implemented Circuit:

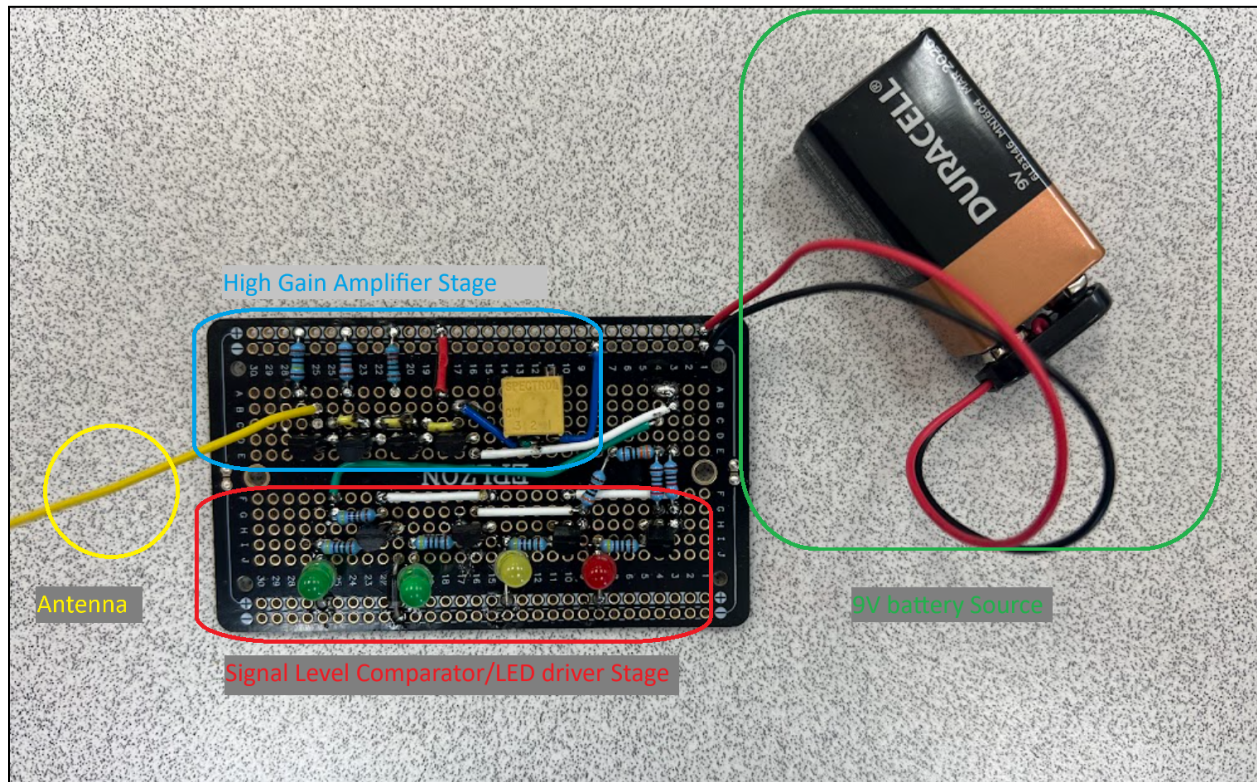


Fig.2

Measurement Results:

Currents through R5, R7, R10 and R11

- $I_{R5} = \sim 0 \text{ A}$
- $I_{R7} = \sim 0 \text{ A}$
- $I_{R10} = \sim 0 \text{ A}$
- $I_{R11} = \sim 0 \text{ A}$

Questions & Considerations:

- How does the circuit detect the electric field strength?
 - The circuit detects electric field strength by using an antenna to capture ambient RF signals, which are then amplified and rectified into a DC voltage that drives LED indicators based on signal intensity.
- How does the circuit indicate the relative field strength?
 - The circuit indicates relative field strength by lighting up a series of LEDs each driven by a transistor that turns on at increasing voltage thresholds so more LEDs light up as the detected signal gets stronger.
- What are the conditions needed to turn on each one of the LEDs?

- Each LED turns on when the amplified RF signal voltage exceeds the specific base-emitter threshold of its corresponding transistor, determined by a resistor network that sets increasing voltage levels for each stage.
- How does the potentiometer VR1 control the sensitivity of the circuit?
 - The potentiometer VR1 controls the sensitivity of the circuit by adjusting the biasing of the amplifier stages, thereby setting the minimum RF signal strength required to trigger the LED indicators.
- How would you change the circuit to increase its sensitivity to atmospheric phenomena?
 - Increasing the gain of the antenna could increase the circuit's sensitivity to atmospheric phenomena.
- How does the circuit performance change when you touch the ground node?
 - It seems unchanged, although this might be related to the length of the antenna, $\lambda/4$ wave antennas require a ground plane.