

EE430 - Electromagnetic Theory and Applications
Project 2: Artificial Lossy Transmission Line
March 3, 2025



- Cameron deLeeuw

Introduction:Objectives:

Implement an artificially lossy transmission line with lumped elements and characterize the line using measurements.

Materials:

Component	No. of items	Value
Capacitor	23	0.047 μ F
Inductor	21	560 μ H
Resistor	4	220 Ohm

Procedure:

The circuit required to create artificially lossy transmission line will consist of capacitors and inductors, each lumped circuit element will be made to create a 'pi' formation. There will be 20 sections in series to create the transmission line.

Images:

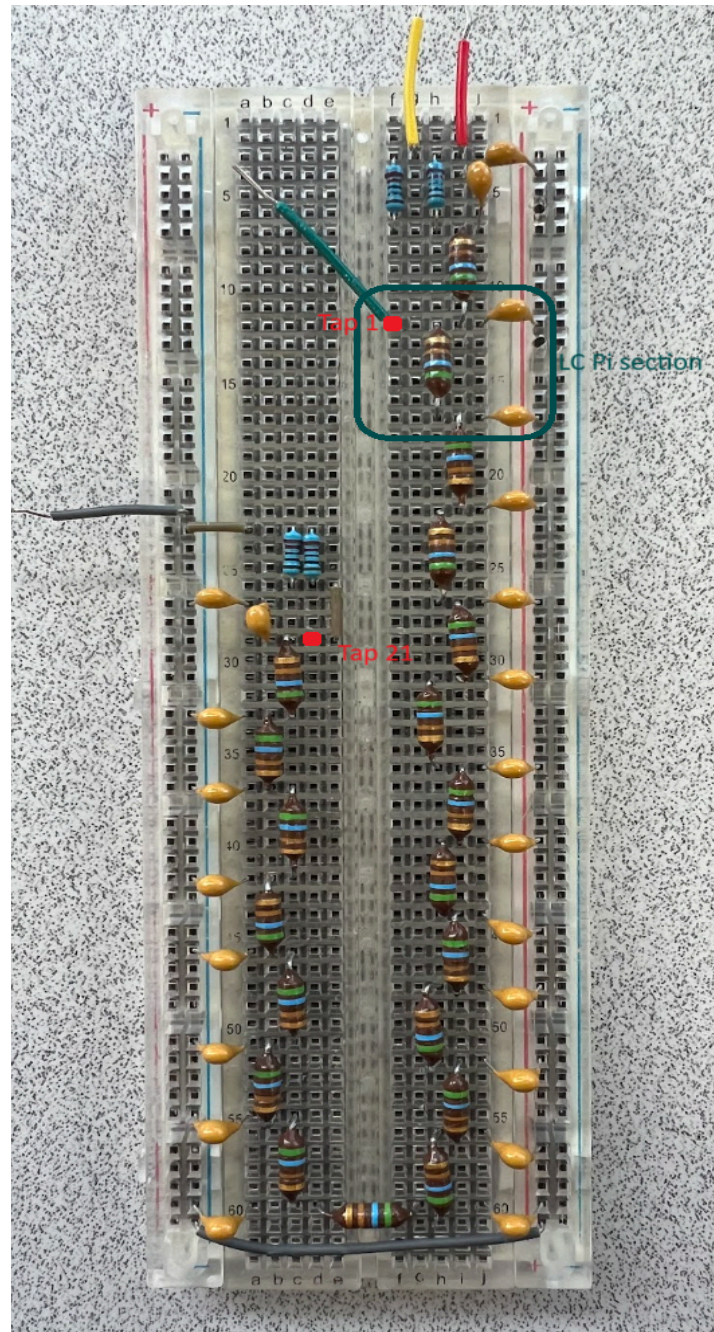


Fig. 1

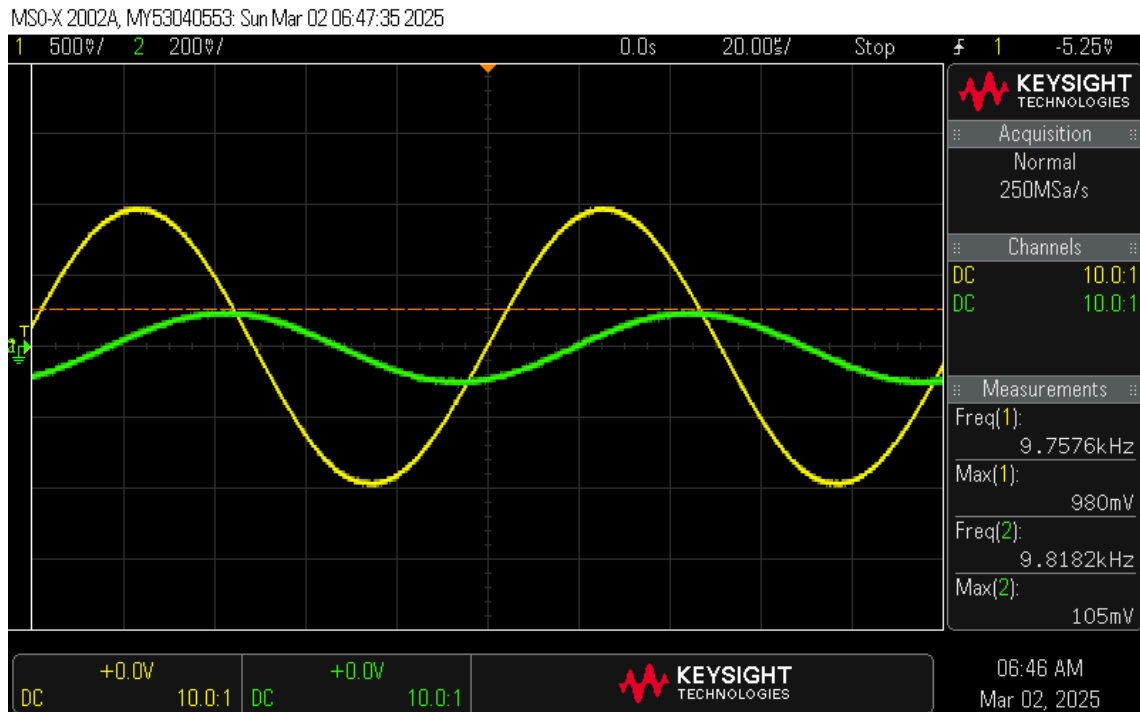


Fig. 110 Ohm load

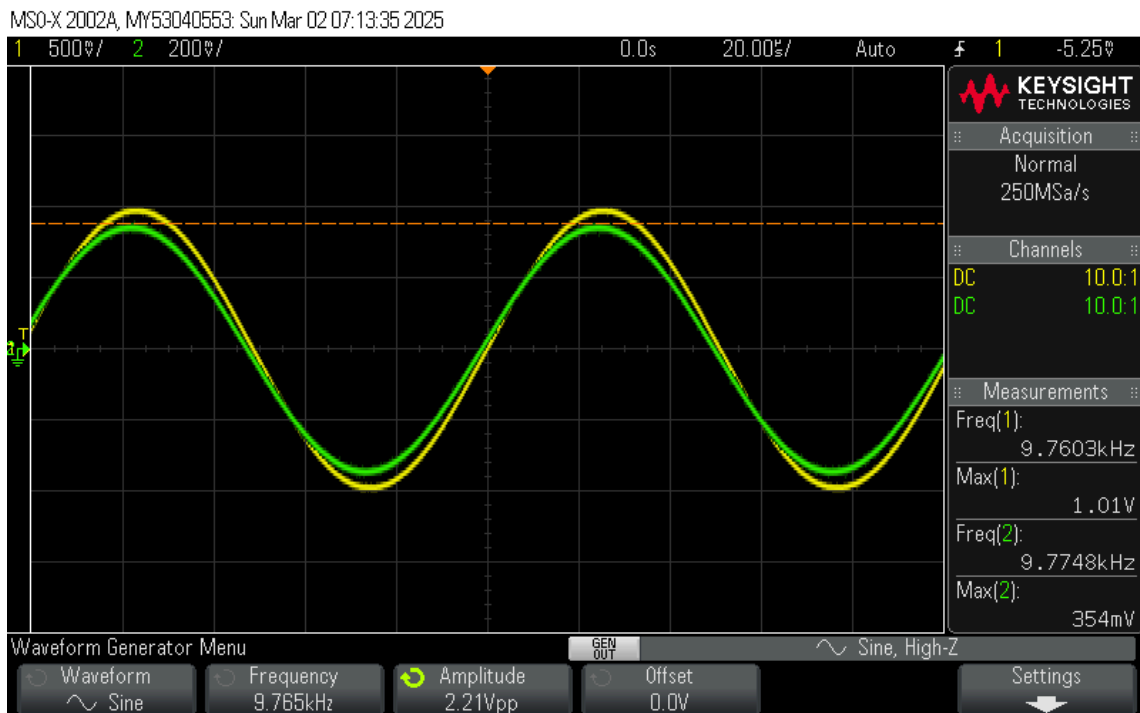


Fig. 3 Open load

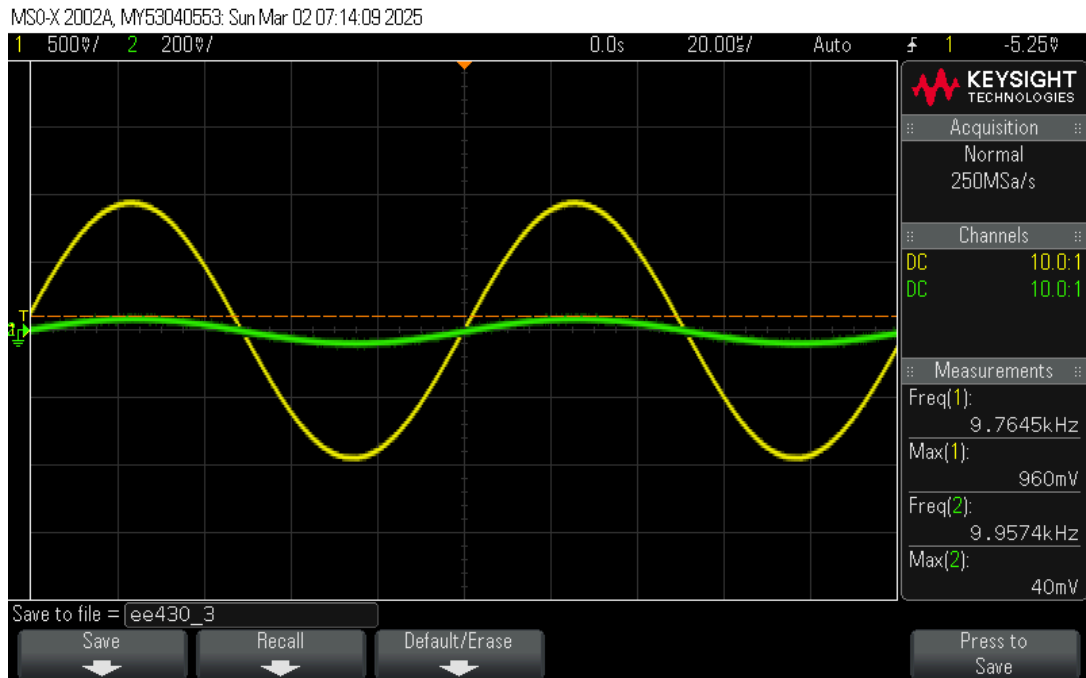


Fig. 4 Shorted load

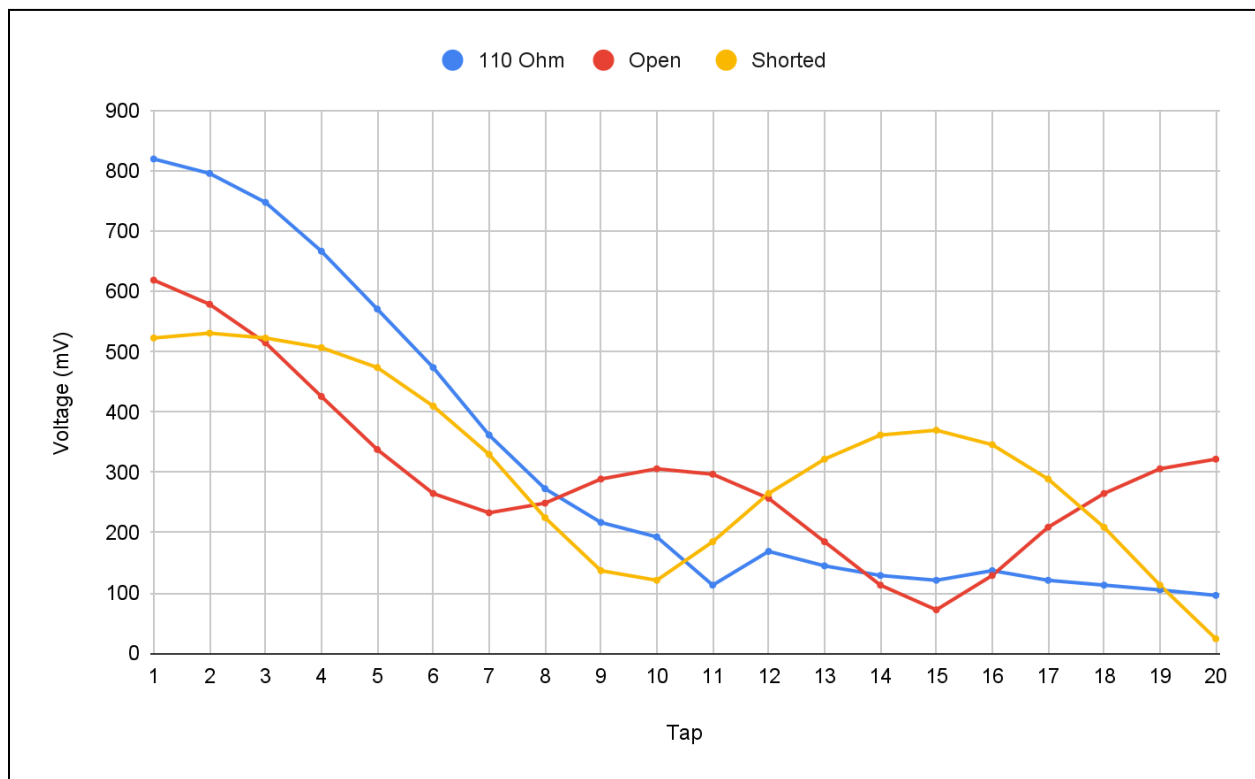


Fig. 5 Voltage amplitude of all taps

Calculations:

Characteristic Impedance:

$$Z_o = \sqrt{\frac{L}{C}}$$

$$Z_o = \sqrt{\frac{560 \times 10^{-6}}{0.047 \times 10^{-6}}}$$

$$Z_o = 109.155 \, \Omega$$

Phase Constant:

$$\beta = \omega \sqrt{LC}$$

$$\beta = 2\pi * 9765 * \sqrt{(560 \times 10^{-6})(0.047 \times 10^{-6})}$$

$$\beta = 0.314 \, rad/m$$

Attenuation Constant:

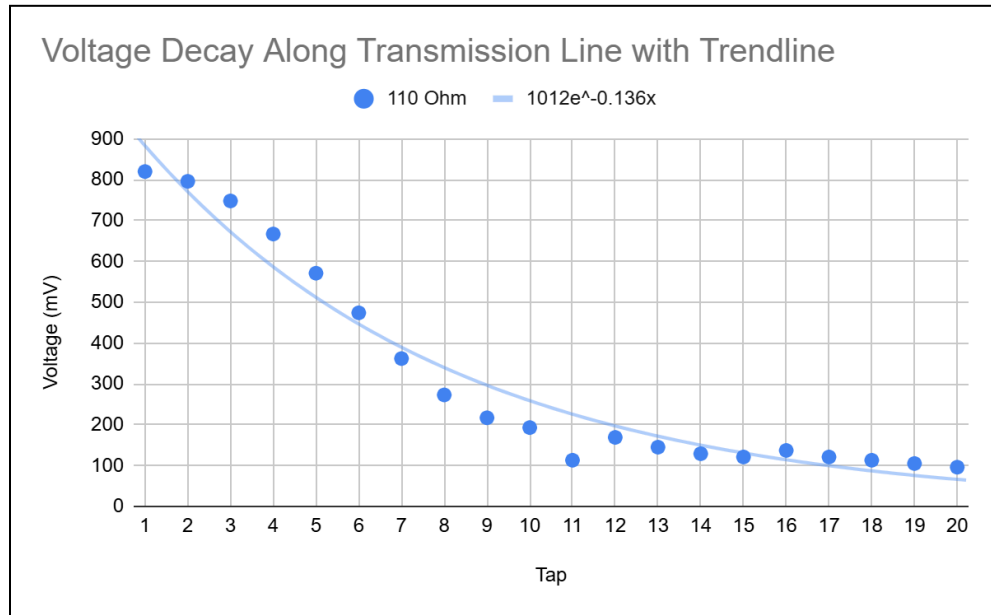


Fig. 6

According to the trendline in Fig. 6, we can see the attenuation constant of each tap is 0.136 Np/tap.

To obtain Np/m we can divide the attenuation per tap by the distance between the taps:

The distance between between separate breadboard holes = 2.54 mm

The distance between separate taps = 5 breadboard holes

$$\alpha (Np/m) = \frac{\alpha (Np/tap)}{d}$$

$$\alpha (Np/m) = \frac{0.136}{5 * 0.00254}$$

$$\alpha = 10.71 \text{ Np/m}$$