EE430 Electromagnetism Project 4: Metal detector April 21, 2025



- Cameron deLeeuw

Schematic:

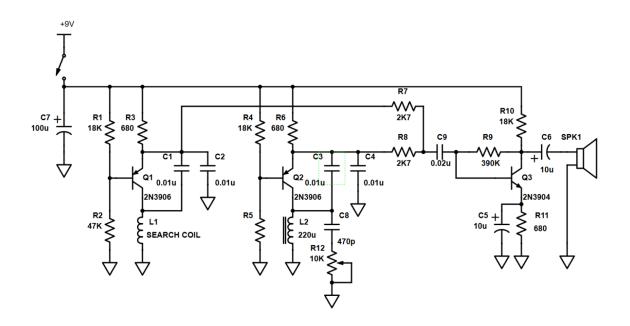


Photo:

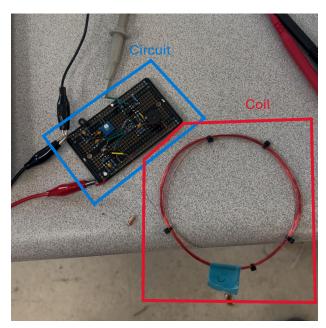



Fig. 1


Theoretical estimate of the search coil inductance based on the beat frequency:

From search coil LC oscillator, f=158050 Hz.


$$L = \frac{1}{(2\pi \cdot 158050)^2 \cdot 5 \times 10^{-9}} \approx 202.5 \mu H$$

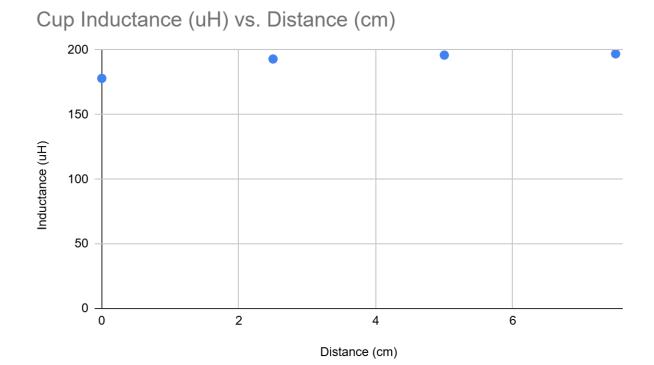Plots of the search coil inductance versus metallic object distance:




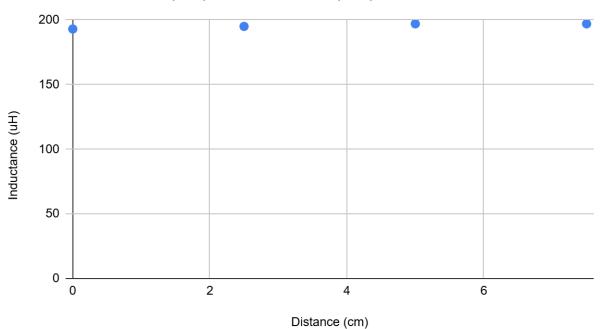

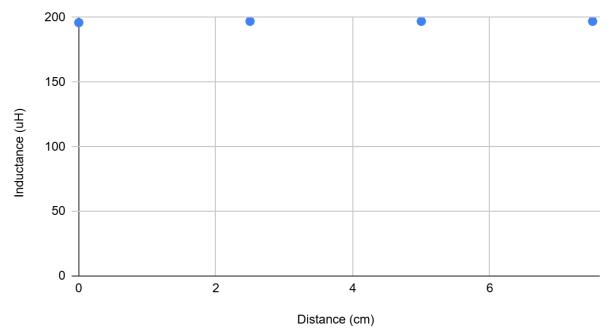Wire stripper Inductance (uH) vs. Distance (cm)




Knife Inductance (uH) vs. Distance (cm)

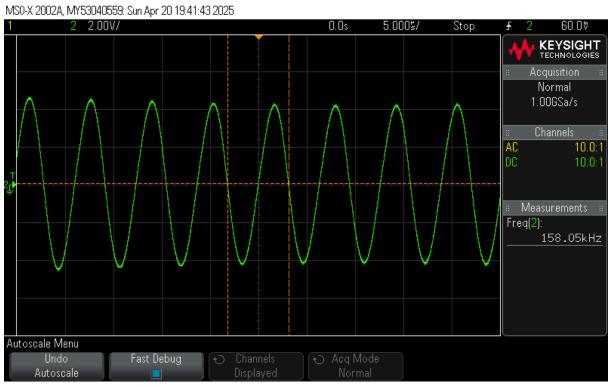

Oscilloscope captures of the oscillators frequency measurement:



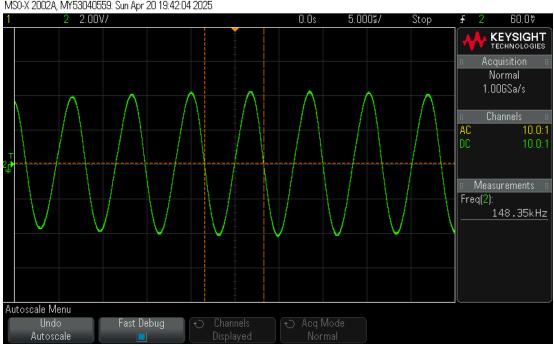





MS0-X 2002A, MY53040559: Sun Apr 20 19:43:04 2025


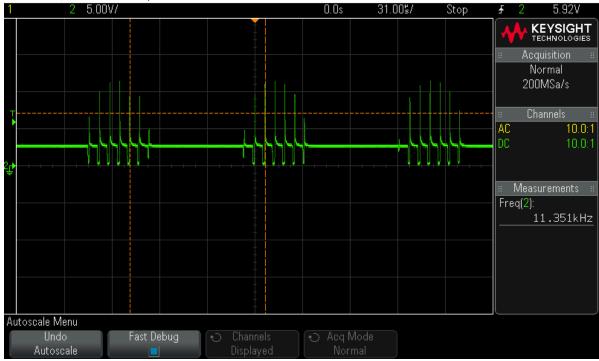


Fig. 4

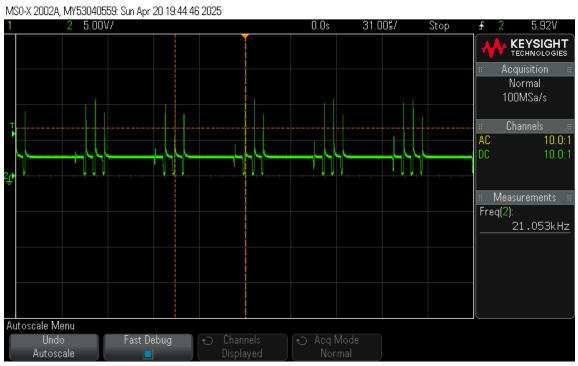

Oscilloscope captures of the beat frequency measurement for different objects:

Fig. 5 Cup

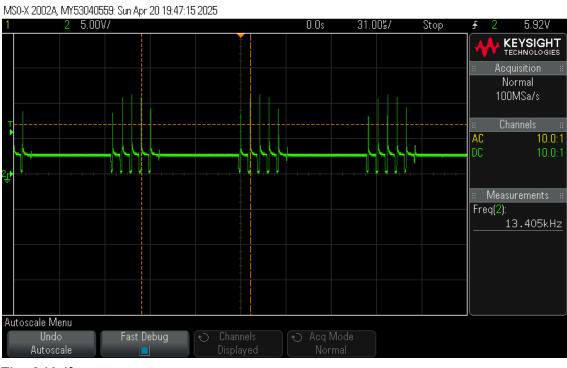


Fig. 6 Knife

Tabulated measurements of beat frequency vs distance for each object:

cup		Knife		Wire Stripper	
Distance (cm)	Beat Fq. (kHz)	Distance (cm)	Beat Fq. (kHz)	Distance (cm)	Beat Fq. (kHz)
0	21	0	13.4	0	11.377
2.5	14.7	2.5	12.3	2.5	11.3
5	12.2	5	11.36	5	11.2
7.5	11.36	7.5	11.36	7.5	11.2